

Boolean Algebra And Logic Gates

Binary

 $0 \rightarrow \text{Off} \rightarrow F \rightarrow 0 \text{ volts}$ $1 \rightarrow \text{ON} \rightarrow T \rightarrow 5 \text{ volts (anything but not zero)}$

WHEN DEALING WITH CIRCUITS (0)

When dealing with Circuits Zero corresponds to being in the off state and 1 (one) corresponds to being in the ON state

WHEN DEALING WITH TRUTH TABLE

0 corresponds to F (false)


1 corresponds to T (true)

WHEN DEALING WITH VOLTAGE

An OFF state will have 0 volts

An ON state will represent something other than ZERO


1) BUFFER GATE

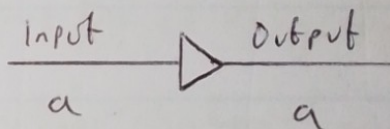

(Whatever a (input) is, a (output) will be the same)


A (input)	Out (output)
1	1
0	0

2) NOT GATE

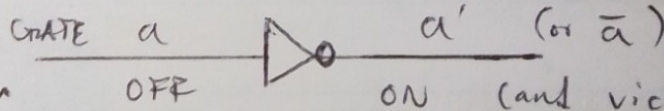


a (input)	Out (output)
0	1
1	0

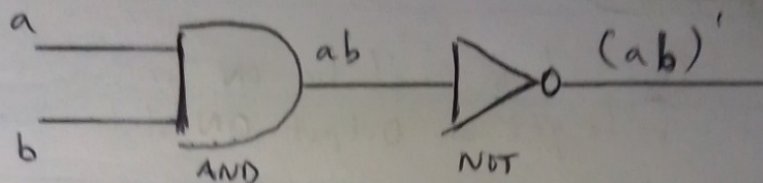
The Combination of a ~~NOR~~ AND GATE & a NOT GATE produces a NAND GATE



EQUAL TO

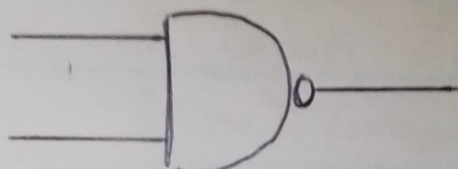

A NAND GATE

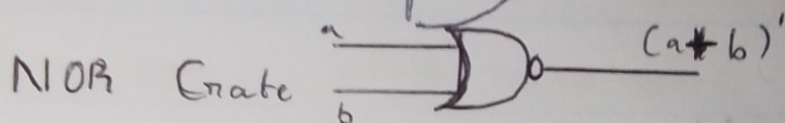

OR $\begin{matrix} a \\ b \end{matrix} \rightarrow a+b$			NOR $\begin{matrix} a \\ b \end{matrix} \rightarrow (a+b)'$		
a	b	a+b	a	b	(a+b)'
0	0	0	0	0	1
1	0	1	1	0	0
0	1	1	0	1	0
1	1	1	1	1	0

NOTE


AND = multiplication

e.g. $\begin{matrix} a \\ b \end{matrix} \rightarrow ab$


OR = Addition

e.g. $\begin{matrix} a \\ b \end{matrix} \rightarrow a+b$

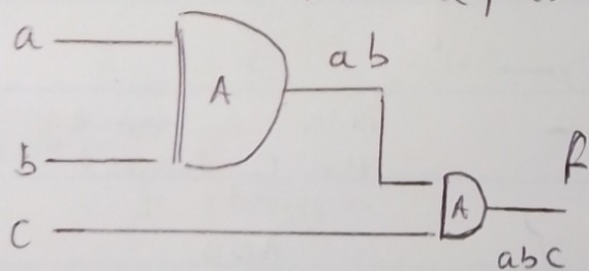Question 1. Write a function using the block diagrams shown below





Ans: $f = abc$

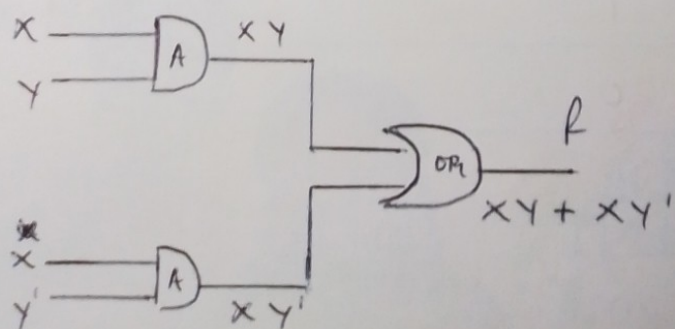

Ans: $f = xy + xy'$

Exercise

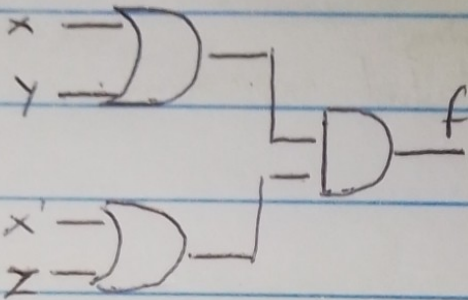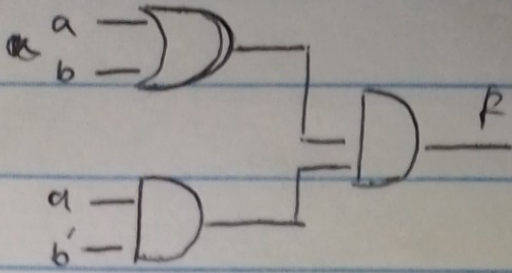


Don't forget

AND = \times (multiplication)

OR = $+$ (Addition)

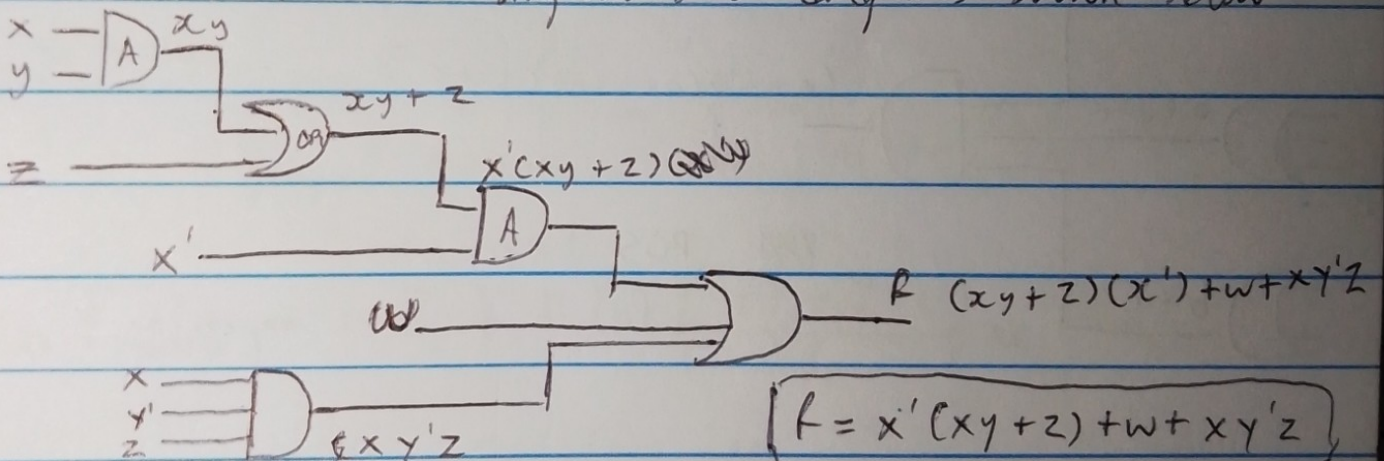
2. Write a function using the block diagrams shown below:



3. Draw a block diagram given the function below:

$$f = ab + c$$

AND OR

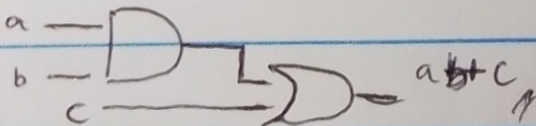

BOSEDE MARY & BAYODE VINCENT


ON SATURDAY 26TH MAY, 2018

COURTESY: THE COUPLE



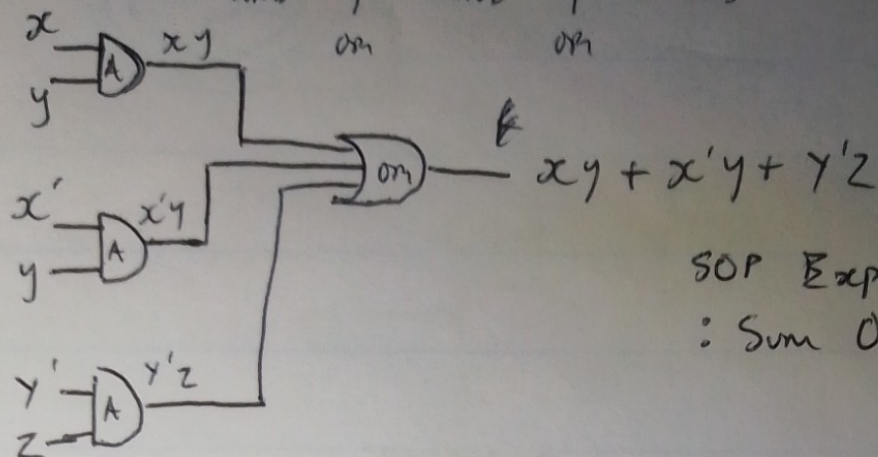
b. Draw a block diagram given the function below

$$f = \underset{\substack{\text{AND} \\ \uparrow \\ \text{OR}}}{xy} + \underset{\substack{\text{AND} \\ \uparrow \\ \text{OR}}}{x'y} + \underset{\substack{\text{AND} \\ \uparrow \\ \text{OR}}}{y'z}$$



SOP Expressing
: Sum Of Product expression

c. $f = (a+b')(a+b+c)(b'+c')$

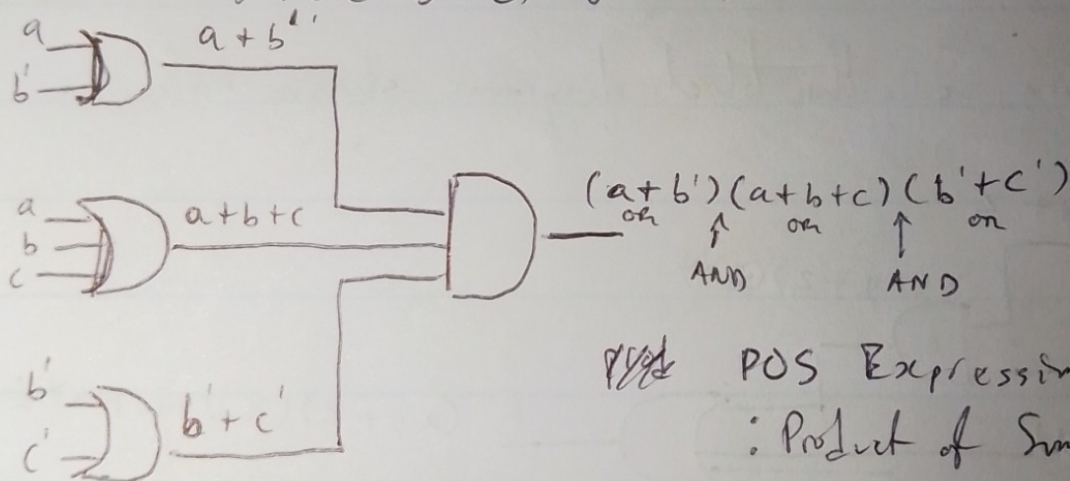

POS Expression
: Product of Sums expression